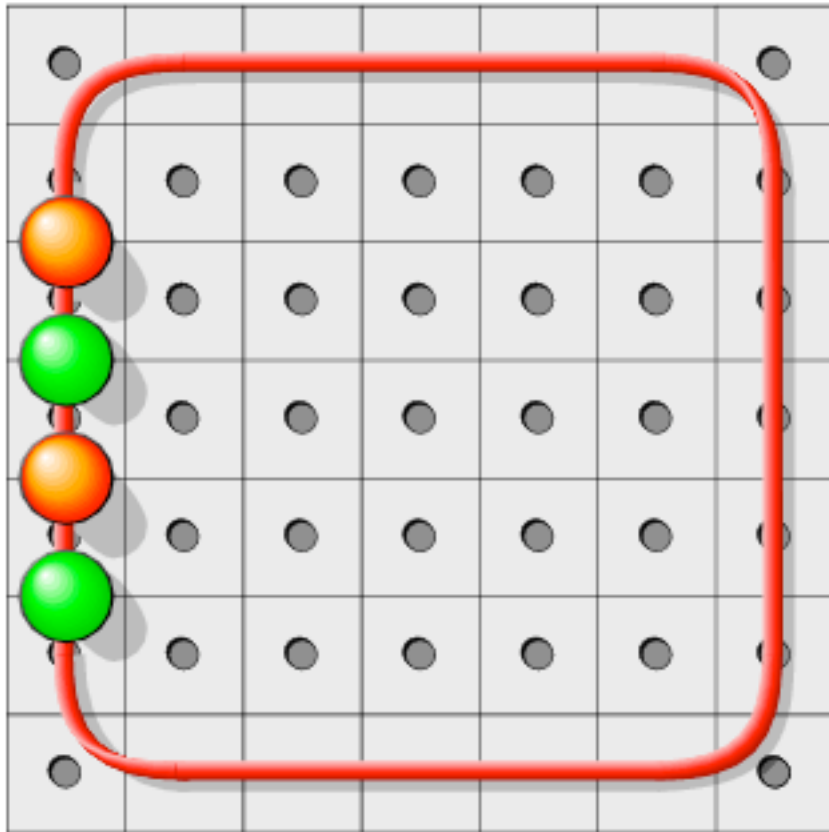


Electricity


Circuit 1



Does this circuit work?

Explain why it will or won't work.

Circuit 2

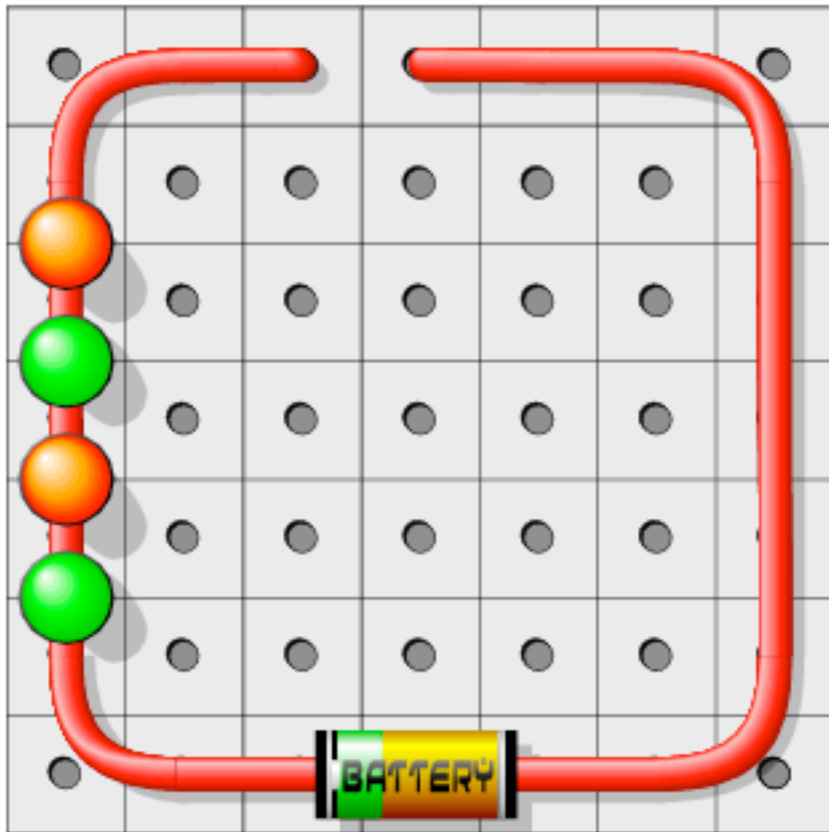

Does this circuit work?

Explain why it will or won't work.