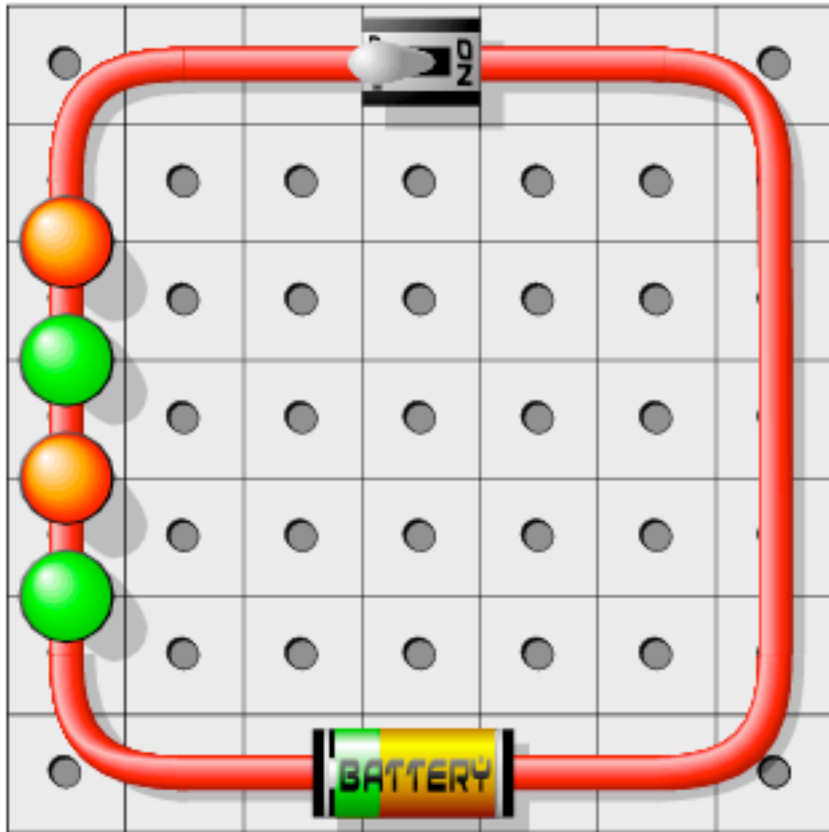


Electricity


Circuit 3



Does this circuit work?

Explain why it will or won't work.

Circuit 4

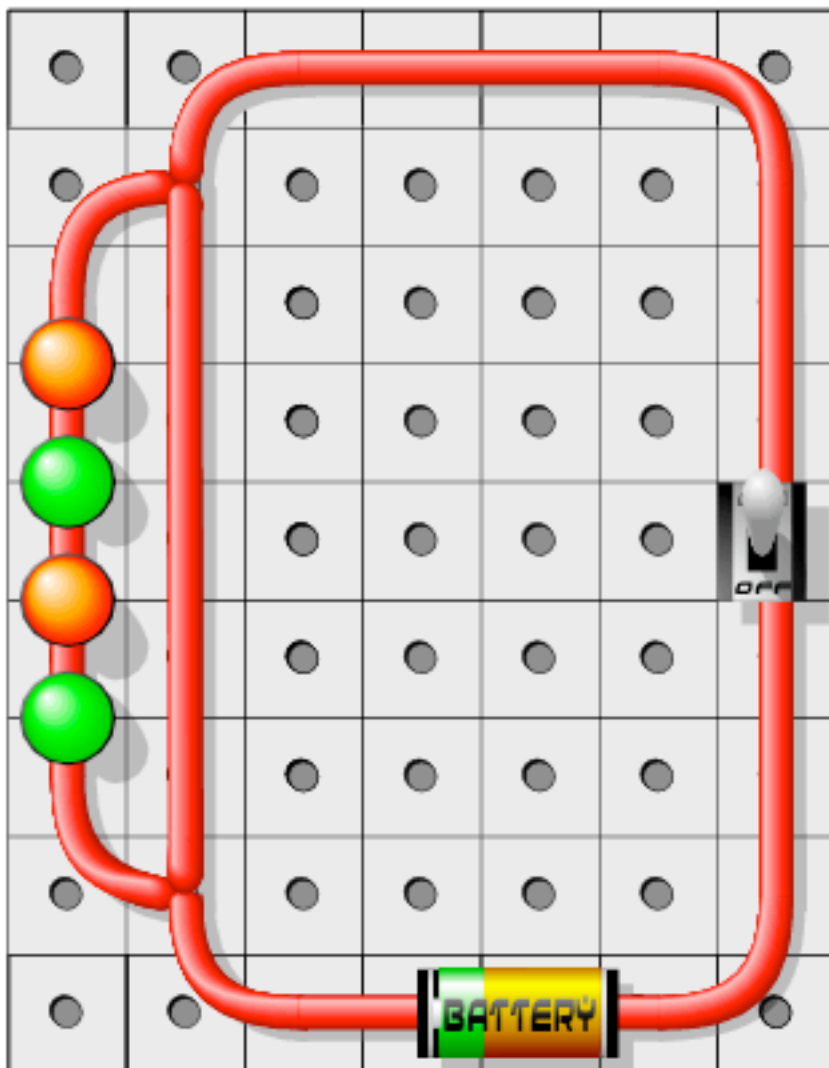

Does this circuit work?

Explain why it will or won't work.